

<Part F>


Reduce the K-map by grouping the 1's and produce optimized equations:

$S =$

$CO =$

<Part G>

 Using the equation draw the Logics for S and Co:



<Part D>

Create Truth Table

What do you think the figure 1 logic is for?

**Table 1: Truth Table**

A	B	Ci	S	Co

<Part E>

Fill in the K-map below:

		AB			
S					
Ci		00	01	11	10
	0				
	1				

		AB			
Co					
Ci		00	01	11	10
	0				
	1				

<Part B>

Change the logic in Figure 1 in terms of NOR gates:

For Example: Buffer can be made with NOR gate with its input tied together.



<Part C>

Change logic design into equations in reduced form:

For Example:  $(A+B) C = AC + BC$

S =

CO =

# Logic Design Worksheet

University of California at Berkeley  
Department of Electrical Engineering and Computer Science  
GRE Preparation Session

Group Tutor: Young H. Cho

Handout 2

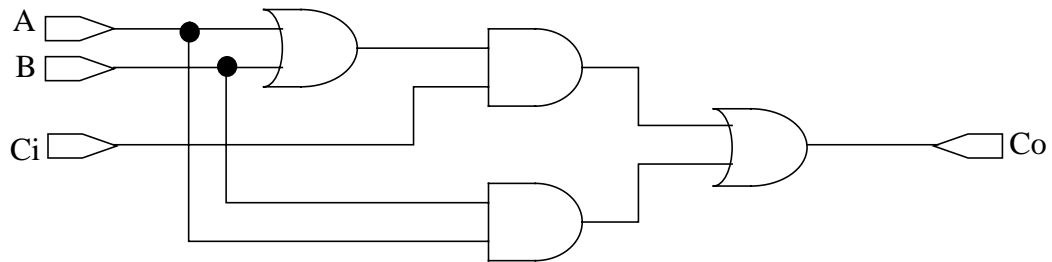
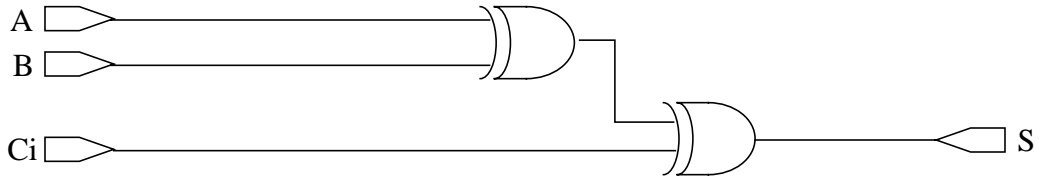


Figure 1: Questions A - E

## Logic Design

<Part A>

Change the logic in Figure 1 in terms of NAND gates:

For Example: Inverter can be made with NAND gate with its input tied together.

